

**CPEN 211 Introduction to Microcomputers, 2018**  
**Lab Proficiency Test #2**


**Question 1 [3 marks]:** Create a file named “q1.v” and inside it write **synthesizable** Verilog that implements the finite state machine illustrated in the figure below. Like the examples in class, state transitions occur on the rising edge of input “clk” and the reset is synchronous (occurs on the rising edge of clk) and is active high (reset equal to 1'b1 means reset). Transitions from a state to itself are not explicitly shown. The condition for an unlabeled edge is always true. The input “in” is 2-bits wide. The output “out” is 3-bits wide. The output for each state is shown in square brackets. For example, when in state A, out should be 001, and if in is 10, then the next state should be B. The auto grader used to mark your answer will assume your top-level module is called “top\_module” with inputs “clk”, “reset” and “in”, output “out”, and that “top\_module” is declared as follows:

```
module top_module(clk,reset,in,out);
```

Your q1.v file **must** include definitions for any modules instantiated inside top\_module (even those from the slides or textbook). **Upload your Verilog file named “q1.v” via the “Lab Proficiency Test #2” assignment on Canvas before 6:50 pm as the submission site closes at exactly 6:50 pm.** Do NOT “zip” your submission. The file you upload for this question **must** be called “q1.v” or the autograder script will not mark it.

Your solution will get zero if any of the following are true:

 1. Your **last** “Lab Proficiency Test #2” attempt on Canvas does not include “q1.v”,
2. Your q1.v file does not compile using ModelSim (e.g., due to syntax errors),
3. Your q1.v file does not contain a module called top\_module with inputs/outputs as above,
4. Your top\_module cannot be simulated (e.g., due to missing module definitions in q1.v),
5. The Verilog used by your top\_module is not synthesizable by Quartus.
6. The Verilog used by your top\_module has any inferred latches.
7. Your top\_module output “out” does not exactly match the output of the state machine below for some sequence of values for inputs “clk”, “reset” and “in”.



**CPEN 211 Introduction to Microcomputers, 2018**  
**Lab Proficiency Test #2**

**Question 2 [3 marks]:** Create a file named “q2.v” and inside it write **synthesizable** Verilog that implements the circuit specified as follows. Your top-level module **must** be called “fab” and have the exact inputs and outputs shown in the lines of code below:

```
module fab(clk, reset, s, in, op, out, done);  
    input clk, reset, s;  
    input [7:0] in;  
    input [1:0] op;  
    output [7:0] out;  
    output done;
```

In module fab write Verilog for a datapath and finite state machine controller that together implement the instructions in the table below:

| Instruction   | Value on input “op” | Operation (may take more than one cycle)   |
|---------------|---------------------|--|
| INIT [1 mark] | 2'b00               | Initialize A to zero, B to one and C to “in”. Copy B to out and set done = 1. A, B and C are 8-bits wide.  |
| FIB [1 mark]  | 2'b01               | Compute sum = “value in A” + “value in B” then, if C is not zero, set A to the prior value of B, set B to sum, and update C to be C – 1. When C equals zero set done = 1 and copy B to out. Use normal (2’s complement) addition for “+” and do NOT take any special actions in case the result A+B overflows. |
| FACT [1 mark] | 2'b10               | If C is not zero, set B = B * C and C = C – 1. When C equals zero set done = 1 and copy B to out. Use the “*” operator in Verilog to compute B * C and use the lower 8-bits of the result when updating B.   |

Your controller should reset to a wait state on the next rising edge of “clk” if “reset” is 1. In the wait state done should be 0. Assume inputs “in”, “op” and “s” are set on the same cycle. Once “s” is set to 1 these inputs will not change until your controller sets “done” to 1. Your controller should stay in the wait state until the input “s” is 1 and there is a rising edge of “clk”. The final value of B computed by the instruction INIT, FIB or FACT should appear on output “out” sometime after “s” is set to 1. When the value on “out” is correct, your controller should set “done” to 1 and then wait for “s” to be set to 0 and a rising edge of clk. Then, your controller should return to the wait state. The autograder will only check the value of out when done is 1. An interface checker is here: [https://cpen211.ece.ubc.ca/2018/lpt-2/q2\\_checker\\_xw8.html](https://cpen211.ece.ubc.ca/2018/lpt-2/q2_checker_xw8.html) (you may need to type out this URL if clicking or cutting and pasting doesn’t work). Ensure “q2\_check\_tb” prints “INTERFACE OK”. The q2\_check\_tb testbench includes simple tests for INIT, FIB and FACT. The autograder will try additional test cases. **Inferred latch and/or synthesis errors in Quartus will result in up to 2 marks deducted for Question 2.** Your q2.v file **must** include definitions for any modules instantiated inside fab. Upload “q2.v” via “Lab Proficiency Test #2” on Canvas **before** 6:50 pm.

**WARNING:** Remember to include “q1.v” when submitting “q2.v” on Canvas. To do this, in the “File Upload” area on Canvas click on [+ Add another file](#) so that you can upload two files. **DO NOT** “zip” your “.v” files before submission. If you resubmit q1.v and/or q2.v and Canvas renames the new files to “q1-N.v” or “q2-N.v”, where N is an integer this is OK.